

Name: _____


7.2 Kirchhoff's Laws

Question for the day: why does our circuit fuse blow up?

We'll need to consider Kirchhoff's Laws first.

Kirchhoff's Current Law states that the total amount of current entering a junction is equal to the total amount of current leaving the junction.

$$I = \frac{Q}{t}$$

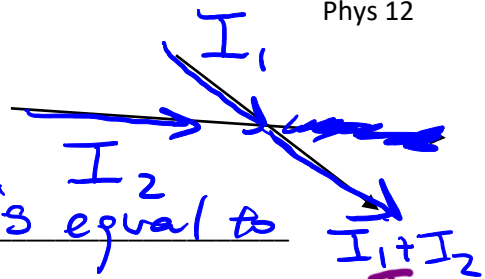

For resistors in **series**, there is only one pathway, so no junctions.

That means the current is the same everywhere in the circuit.

$$I_{Total} = I_1 = I_2 = I_3$$

Since $I = Q/t$, multiplying all the I's by time, t, gives us Q! The charge must also be the same everywhere.

$$Q_{Total} = Q_1 = Q_2 = Q_3$$


For resistors in **parallel**, your current branches off into multiple pathways.

At each junction, the current either splits off or combines. Therefore, the current of each branch, must add up to the total current.

$$I_{Total} = I_1 + I_2 + I_3$$

Therefore, the charge Q:

$$Q_{Total} = Q_1 + Q_2 + Q_3$$

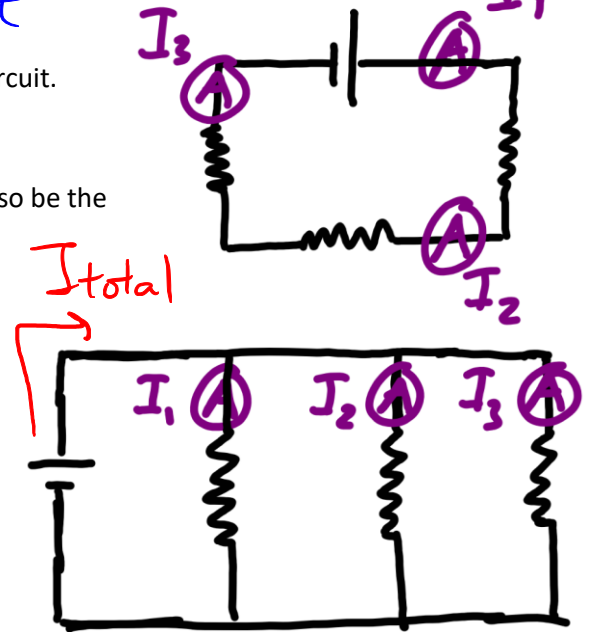


Kirchhoff's Voltage Law states that the sum of the potential differences in a circuit must add up to the total voltage. Otherwise, energy would not be conserved, breaking the law of conservation of energy.

Across a resistor following the direction of the current, you would get a voltage drop. Across a battery/cell following the direction of the current, you would gain voltage.


For resistors in **series**, the potential drop going around the circuit should add up to the total voltage (V_T across the battery)

$$V_{Total} = V_1 + V_2 + V_3$$

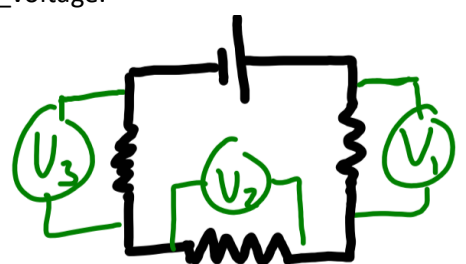


For resistors in **parallel**, since the potential difference drop happens at the same location in your circuit, the potential different across each resistor is the same.

$$V_{Total} = V_1 = V_2 = V_3$$

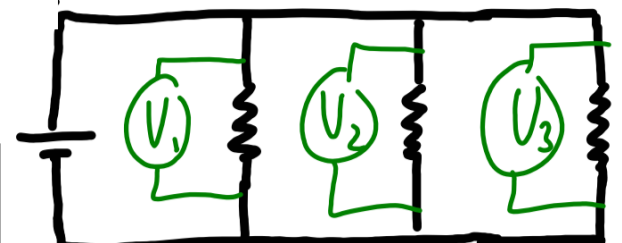

Name: _____

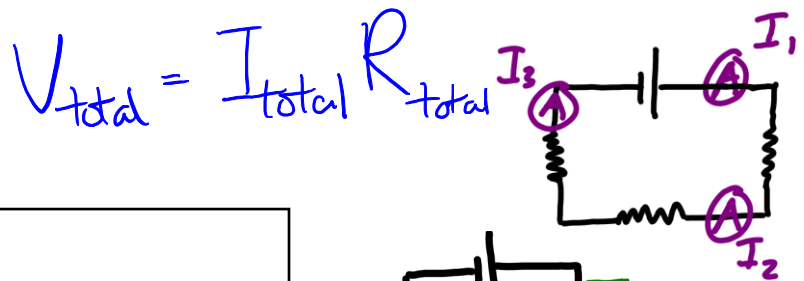
So, how do we calculate the total resistance in a circuit?



For resistors in **series**:

→ $V_{total} = V_1 + V_2 + V_3$

$R_{total} = R_1 + R_2 + R_3$

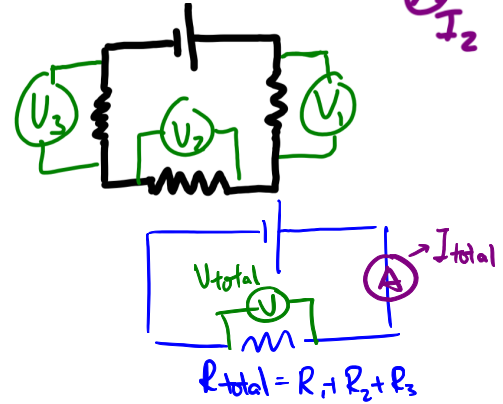


Think of it this way, more resistance in your circuit is like adding more roadblocks while you're driving. As a result, you'll have to drive slower.

For resistors in **parallel**:

$V = IR$

$I_{total} = I_1 + I_2 + I_3$

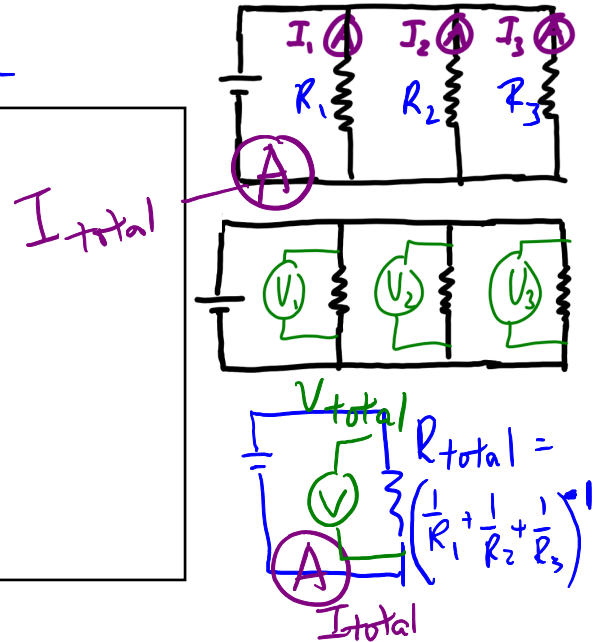$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$



TRY THIS! -> Refer to 7.2 Inquiry Questions

What about capacitors? Why do we connect capacitors in a circuit: _____ surges, _____ control, etc

Capacitors in **series**:

Capacitors in **parallel**:

Why? Try working it out using $Q = CV$, $V_{total} = V_1 + V_2 + V_3$, and $Q_{total} = Q_1 + Q_2 + Q_3$

How do these equations compare with the resistor ones?

HW: Worksheet 6.2 (all) and Inquiry question 6.2 (all)