

Name: _____

Worksheet 6.8 Back EMF *Do on separate sheet of paper.*

1. A 120 V DC motor draws 12.0 A when it reaches its full operating speed. If the resistance of the armature of this motor is 6.0Ω , what is the back emf when it reaches its full operating speed? (48 V)

2. A 120 V motor draws 15.0 A when it reaches its full operating speed and 40.0 A when it is initially turned on. Find.
 - a) The resistance of the armature. (3.00 Ω)
 - b) The back emf when it reaches its full operating speed. (75 V)

3. A 120 V motor draws 9.0 A when it reaches its full operating speed. If the resistance of the armature is 5.0Ω , find.
 - a) The back emf when the motor is operating at full speed. (75 V)
 - b) The back emf when the motor is initially turned on. (0 V)
 - c) The current when the motor is initially turned on. (24 A)

4. The armature of a 120V motor slows down because of an increased load (for example an electric lawn mower enters thick, tall grass). The resistance of the armature is 6.0Ω , and the current drawn by the motor when operating at full speed is 3.6 A. The current drawn by the motor when the increased load is applied is 8.4 A.
 - a) Explain why the motor (armature) gets hotter when the increased load slows it down.
 - b) Explain why the current through the armature increase when the load is increased.
 - c) What is the back emf when
 - i. the motor is operating at full speed. (98 V)
 - ii. the motor slowed down because of the increased load. (70 V)

5. The back emf in a motor is 90.0 V when the armature of the motor is turning at 1000 rev/min. What is the back emf in the same motor when the motor is turning 500 rev/min? (45.0 V)

6. The current drawn by a 120 V motor when the motor is turned on is 10.0 A and 3.0 A when it is operating at its full speed.
 - a) What is the resistance of the armature? (12.0 ohms)
 - b) What is the back emf when the motor is operating at full speed? (84 V)